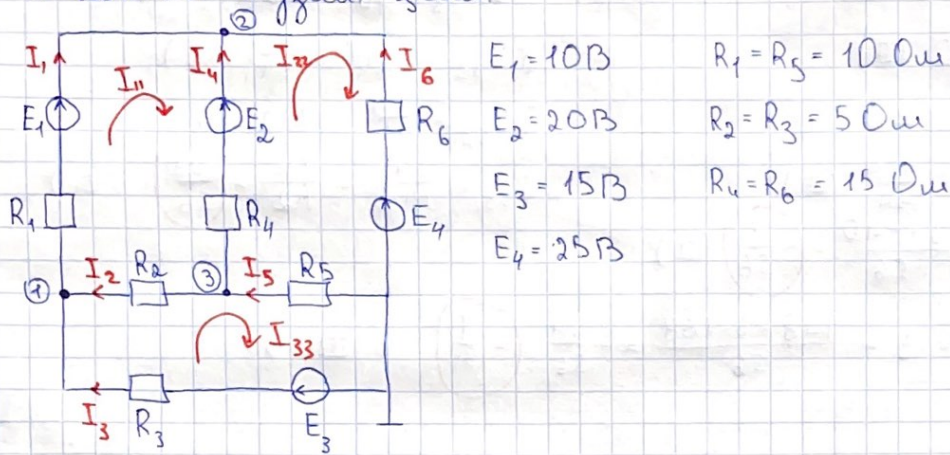


### Задача 1.

Задание: составить систему уравнений по методу контурных токов и методу узл. пот-лов, определить токи в ветвях и токи в узлах цепи.



### Решение:

#### 1. Метод контурных токов.

$$\begin{cases} I_{11}(R_1 + R_4 + R_2) - I_{22} \cdot R_4 - I_{33} \cdot R_2 = E_1 - E_2 \\ I_{22}(R_4 + R_6 + R_5) - I_{11} \cdot R_4 - I_{33} \cdot R_5 = E_2 - E_4 \\ I_{33}(R_2 + R_5 + R_3) - I_{11} \cdot R_2 - I_{22} \cdot R_5 = E_3 \end{cases}$$

$$\begin{cases} I_{11} \cdot 30 - I_{22} \cdot 15 - I_{33} \cdot 5 = -10 \\ I_{22} \cdot 40 - I_{11} \cdot 15 - I_{33} \cdot 10 = -5 \\ I_{33} \cdot 20 - I_{11} \cdot 5 - I_{22} \cdot 10 = 15 \end{cases}$$

$$\begin{cases} I_{11} \cdot 30 - I_{22} \cdot 15 - I_{33} \cdot 5 = -10 \\ I_{22} \cdot 40 - I_{11} \cdot 15 - I_{33} \cdot 10 = -5 \\ I_{33} \cdot 20 - I_{11} \cdot 5 - I_{22} \cdot 10 = 15 \end{cases}$$

$$\begin{cases} I_{11} \cdot 30 - I_{22} \cdot 15 - I_{33} \cdot 5 = -10 \\ I_{22} \cdot 40 - I_{11} \cdot 15 - I_{33} \cdot 10 = -5 \\ I_{33} \cdot 20 - I_{11} \cdot 5 - I_{22} \cdot 10 = 15 \end{cases}$$

$$\begin{cases} 6I_{11} - 3I_{22} - I_{33} = -2 & \text{(I)} \\ -3I_{11} + 8I_{22} - 2I_{33} = -1 & \text{(II)} \\ -I_{11} - 2I_{22} + 4I_{33} = 3 & \text{(III)} \end{cases}$$

$$\begin{cases} 6I_{11} - 3I_{22} - I_{33} = -2 & \text{(I)} \\ -3I_{11} + 8I_{22} - 2I_{33} = -1 & \text{(II)} \\ -I_{11} - 2I_{22} + 4I_{33} = 3 & \text{(III)} \end{cases}$$

$$\begin{cases} 6I_{11} - 3I_{22} - I_{33} = -2 & \text{(I)} \\ -3I_{11} + 8I_{22} - 2I_{33} = -1 & \text{(II)} \\ -I_{11} - 2I_{22} + 4I_{33} = 3 & \text{(III)} \end{cases}$$



$$I_{11} = -2I_{22} + 4I_{33} - 3 \quad (\text{III})$$

$$-3I_{11} = 6I_{22} - 12I_{33} + 9 \quad (3 \cdot \text{III})$$

$$6I_{22} - 12I_{33} + 9 + 8I_{22} - 2I_{33} = -1 \quad (\text{II})$$

$$14I_{22} - 14I_{33} + 10 = 0 \quad (\text{II})$$

$$I_{22} - I_{33} + \frac{10}{14} = 0 \quad (\text{II})$$

$$I_{22} = I_{33} - \frac{10}{14} \quad (\text{II})$$

$$-15I_{22} = -15I_{33} + \frac{150}{14} \quad (\text{II})$$

$$I_{22} = \frac{37}{56} - \frac{10}{14} = \frac{37-40}{56} = -\frac{3}{56} \quad (\text{II})$$

$$I_{11} = \frac{6}{56} + \frac{4 \cdot 37}{56} - 3 = \frac{148+6-168}{56} = -\frac{14}{56} = -\frac{1}{4} \quad (\text{III})$$

$$\text{Terga: } I_{11} = -\frac{1}{4}, \quad I_{22} = -\frac{3}{56}, \quad I_{33} = \frac{34}{56}$$

$$I_1 = I_{11} = -\frac{1}{4} \text{ A}$$

$$I_2 = I_{11} - I_{33} = \frac{-14-37}{56} = -\frac{51}{56} \text{ A}$$

$$I_3 = I_{33} = \frac{37}{56} \text{ A}$$

$$I_4 = -I_{11} + I_{22} = \frac{11}{56} \text{ A}$$

$$I_5 = I_{22} - I_{33} = -\frac{5}{7} \text{ A}$$

$$I_6 = -I_{22} = \frac{3}{56} \text{ A}$$

$$6I_{11} = -12I_{22} + 24I_{33} - 18 \quad (\text{III})$$

$$-12I_{22} + 24I_{33} - 18 - 3I_{22} - I_{33} = -2 \quad (\text{I})$$

$$-15I_{22} + 23I_{33} = 16 \quad (\text{I})$$

$$-15I_{33} + \frac{150}{14} + 23I_{33} = 16 \quad (\text{I})$$

$$8I_{33} = \frac{224}{14} - \frac{150}{14} \quad (\text{I})$$

$$8I_{33} = \frac{74}{14} \quad (\text{I})$$

$$I_{33} = \frac{74}{14 \cdot 8} = \frac{74}{112} = \frac{37}{56} \quad (\text{I})$$



## 2. Метод узловых потенциалов.

$$U_k \sum_{i=1}^n G_{ki} - \sum_{i=1}^n U_i G_{ki} = \sum_{i=1}^n E_{ki} G_{ki}$$

- $U_k$  - пот. узла, отн. которому составлено ур-ие
- $G_{ki}$  - проводимость ветвей, соединяющих этот узел с сосед. узлами
- $U_i$  - пот. сосед. узлов
- $E_{ki}$  - э.д.с. в ветвях ветвей (знак "+", если э.д.с. направлена к узлу)

$$\begin{cases} U_1 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - U_2 \cdot \frac{1}{R_1} - U_3 \cdot \frac{1}{R_2} = -E_1 \cdot \frac{1}{R_1} + E_3 \cdot \frac{1}{R_3} \\ U_2 \left( \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_6} \right) - U_1 \cdot \frac{1}{R_1} - U_3 \cdot \frac{1}{R_4} = E_1 \cdot \frac{1}{R_1} + E_2 \cdot \frac{1}{R_4} + E_4 \cdot \frac{1}{R_6} \\ U_3 \left( \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right) - U_1 \cdot \frac{1}{R_2} - U_2 \cdot \frac{1}{R_4} = -E_2 \cdot \frac{1}{R_4} \end{cases}$$

$$\begin{cases} \frac{1}{2} U_1 - \frac{1}{10} U_2 - \frac{1}{5} U_3 = 2 & (I) \end{cases}$$

$$\begin{cases} -\frac{1}{10} U_1 + \frac{7}{30} U_2 - \frac{1}{15} U_3 = 4 & (II) \end{cases}$$

$$\begin{cases} -\frac{1}{5} U_1 - \frac{1}{15} U_2 + \frac{11}{30} U_3 = -\frac{4}{3} & (III) \end{cases}$$

$$\begin{cases} 5U_1 - U_2 - 2U_3 = 20 & (I) \end{cases}$$

$$\begin{cases} -3U_1 + 7U_2 - 2U_3 = 120 & (II) \end{cases}$$

$$\begin{cases} -6U_1 - 2U_2 + 11U_3 = -40 & (III) \end{cases}$$

$$u_2 = 5u_1 - 2u_3 - 20 \quad (I)$$

$$-2u_2 = -10u_1 + 4u_3 + 40 \quad (I)$$

$$-6u_1 - 10u_1 + 4u_3 + 40 + 11u_3 = -40 \quad (III)$$

$$-16u_1 + 15u_3 = -80 \quad (III)$$

$$-16u_1 = -80 - 15u_3 \quad (III)$$

$$u_1 = 5 + \frac{15}{16}u_3 \quad (IV)$$

$$-3u_1 = -15 - \frac{45}{16}u_3 \quad (III)$$

$$-15 - \frac{45}{16}u_3 + 35 + \frac{301}{16}u_3 - 2u_3 = 120 \quad (II)$$

$$\frac{-45 + 301 - 32}{16}u_3 = 100 \quad (II)$$

$$\frac{224}{16}u_3 = 100 \quad (II)$$

$$14u_3 = 100 \quad (II)$$

$$u_3 = \frac{100}{14} \quad (II)$$

$$7u_2 = 35u_1 - 14u_3 - 140 \quad (I)$$

$$7u_2 = 175 + \frac{525}{16}u_3 - 14u_3 - 140 \quad (I)$$

$$7u_2 = 35 + \frac{301}{16}u_3 \quad (I)$$

$$35u_1 = 175 + \frac{525}{16}u_3 \quad (III)$$

$$u_1 = 5 + \frac{15}{16} \cdot \frac{100}{14} \quad (III)$$

$$u_1 = \frac{655}{56} \quad (III)$$

$$u_2 = \frac{5 \cdot 655}{56} - \frac{200}{14} - 20 = \frac{1355}{56}$$

Answer:

$$1) \quad I_1 = -\frac{1}{4}A, \quad I_2 = -\frac{51}{56}A, \quad I_3 = \frac{37}{56}A, \quad I_4 = \frac{11}{56}A, \quad I_5 = -\frac{5}{7}A, \quad I_6 = \frac{3}{56}A$$

$$2) \quad u_1 = \frac{655}{56}B \approx 11.7B, \quad u_2 = \frac{1355}{56}B \approx 24.2B, \quad u_3 = \frac{100}{14}B \approx 7.1B$$